

Circuits –Test Review

1. Compare the resistance of branch 1 with that of branch 2. A branch is a section of a circuit. The resistance of branch 1 is _____ branch 2.

(A) Four times

(B) Double


(C) The same as

(D) Half

(E) One quarter (1/4)



Branch 1

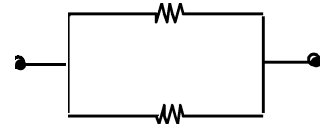

Branch 2

2. Compare the brightness of bulb A with bulb B. Bulb A is _____ bright as bulb B.



(A) One fourth (1/4) as

(B) Half as

(C) Equally

(D) Twice as

(E) Four times as

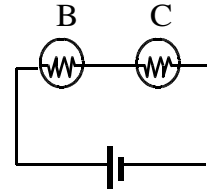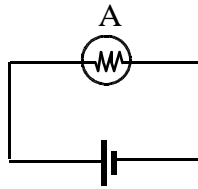

3. What happens to the potential difference (ΔV) between points 1 and 2 when the switch is closed?


(A) Quadruples (4 times)

(B) Doubles

(C) Stays the same


(D) Reduces by half

(E) Reduces by one quarter (1/4)

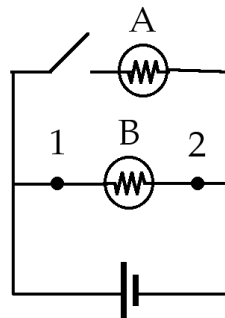


4. Arrange the schematic diagrams below in order of increasing equivalent resistance.

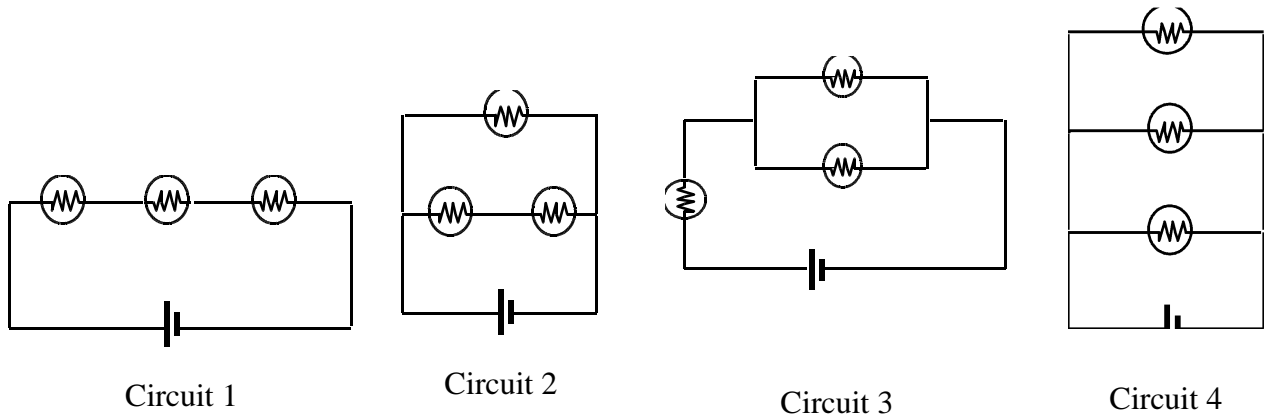- (A) 1, 2, 3, 4
- (B) 4, 3, 2, 1
- (C) 4, 2, 3, 1
- (D) 1, 3, 2, 4




5. What happens to the brightness of the bulbs when the switch is **opened**?

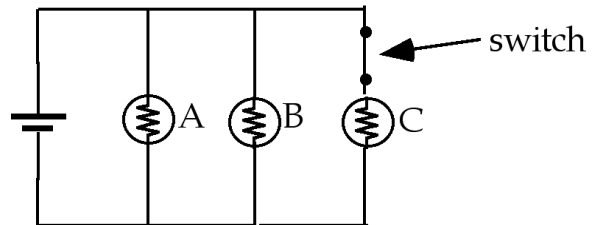- (A) all 3 bulbs go out
- (B) A and B get dimmer, C goes out
- (C) A and B get brighter, C goes out
- (D) A and B remain the same, C goes out
- (E) A is brighter than B, C goes out




6. Compare the brightness of bulb A with bulb B. Bulb A is _____ bright as Bulb B.


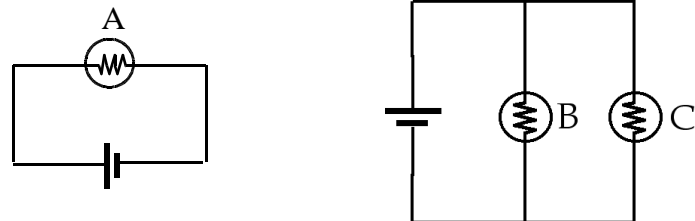
- (A) Four times as
- (B) Twice as
- (C) Equally as
- (D) Half as
- (E) One fourth (1/4) as



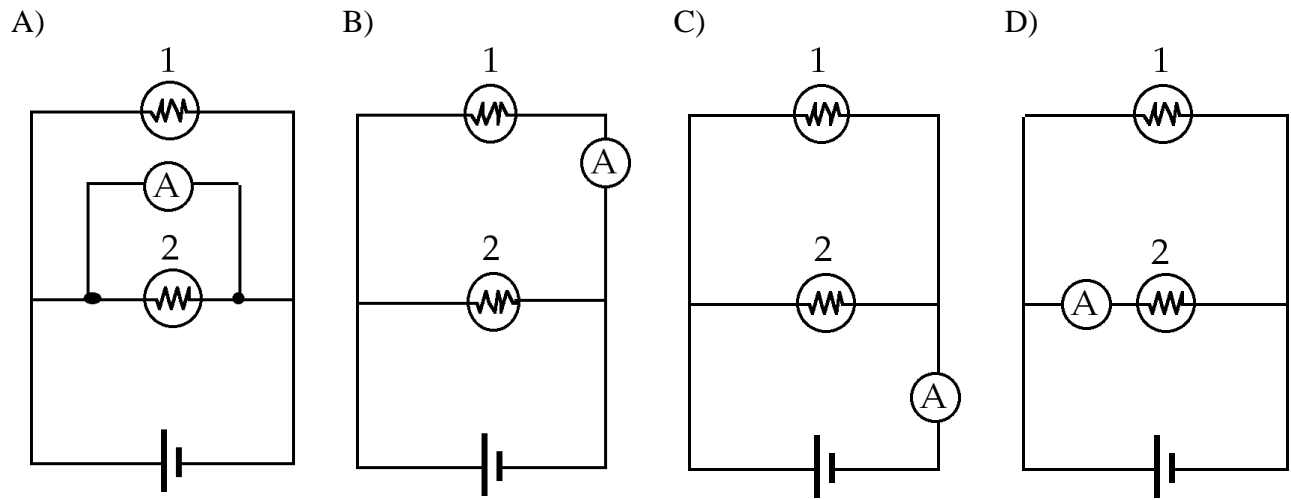7. Which diagram shows the proper placement of an ammeter to measure the current through bulb 2?



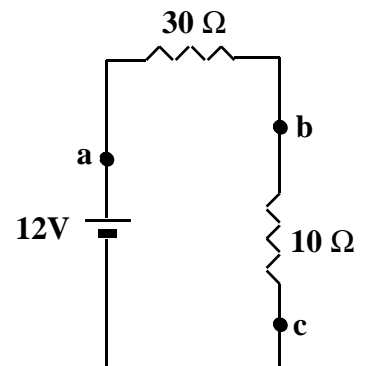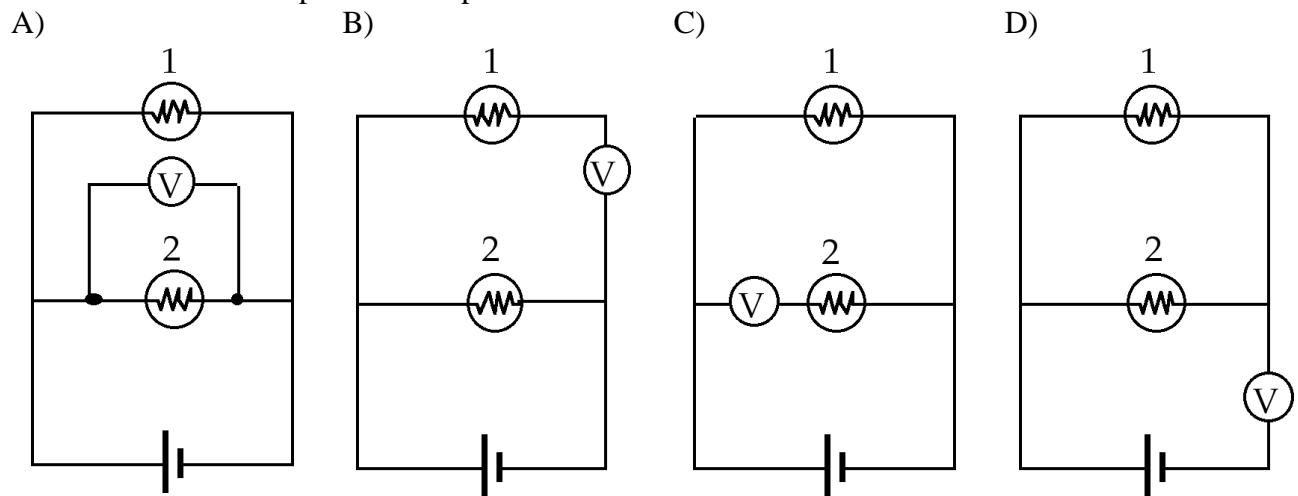8. Which diagram shows the proper placement of a voltmeter to measure the potential drop across bulb 2?



9. Consider the circuit at right. Determine

- a. the potential drop from a to b.

- b. the current flowing through point c.

- c. the power dissipated by the $10\ \Omega$ resistor.